

Assignment 12


DESABOINA SRI SATHWIK-AI24BTECH11007

GATE-2024:EE

- 1) A 3-phase, 11 kV, 10 MVA synchronous generator is connected to an inductive load of power factor $\frac{\sqrt{3}}{2}$ via a lossless line with a per-phase inductive reactance of 5Ω . The per-phase synchronous reactance of the generator is 30Ω with negligible armature resistance. If the generator is producing the rated current at the rated voltage, then the power factor at the terminal of the generator is
(EE:2024)

a) 0.63 lagging. b) 0.87 lagging. c) 0.63 leading. d) 0.87 leading.

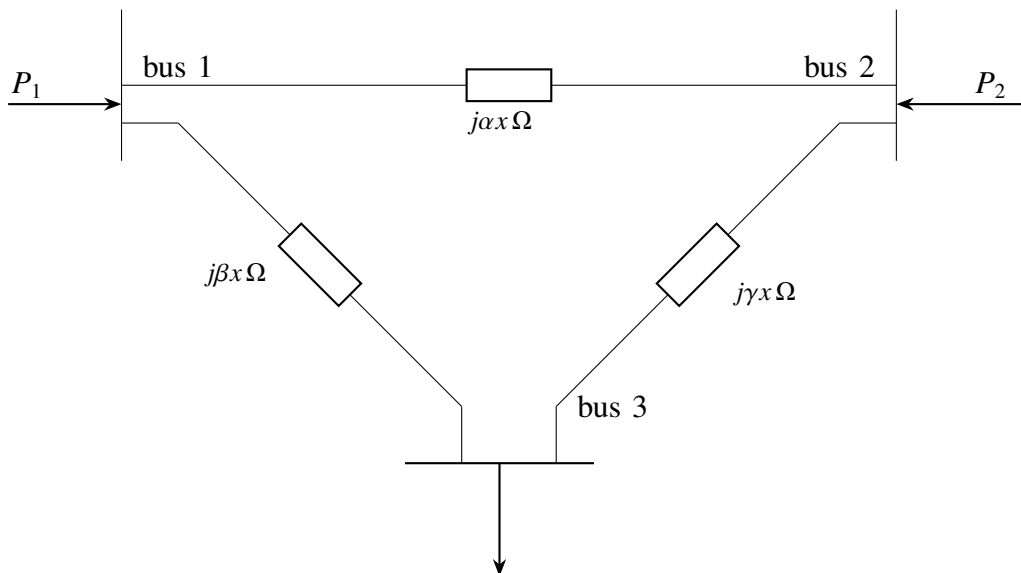- 2) For the three-bus lossless power network shown in the figure, the voltage magnitudes at all the buses are equal to 1 per unit (pu), and the differences of the voltage phase angles are very small. The line reactances are marked in the figure, where α, β, γ , and x are strictly positive. The bus injections P_1 and P_2 are in pu . If $P_1 = mP_2$, where $m > 0$, and the real power flow from bus 1 to bus 2 is $0 pu$, then which one of the following options is correct?




(EE:2024)

a) $\gamma = m\beta$ b) $\beta = m\gamma$ c) $\alpha = m\gamma$ d) $\alpha = m\beta$

- 3) A BJT biasing circuit is shown in the figure, where $V_{BE} = 0.7 V$ and $\beta = 100$. The Quiescent Point values of V_{CE} and I_C are respectively

(EE:2024)

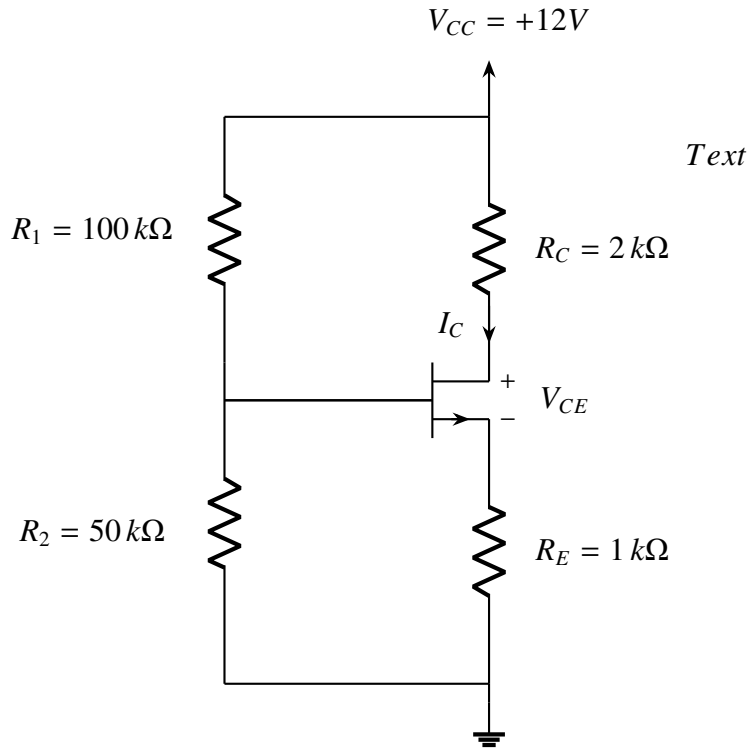

- a) 4.6 V and 2.46 mA c) 2.61 V and 3.13 mA
b) 3.5 V and 2.46 mA d) 4.6 V and 3.13 mA

4) Let $f(t)$ be a real-valued function whose second derivative is positive for $-\infty < t < \infty$. Which of the following statements is/are always true?

(EE:2024)

- a) $f(t)$ has at least one local minimum.
b) $f(t)$ cannot have two distinct local minima.
c) $f(t)$ has at least one local maximum.
d) The minimum value of $f(t)$ cannot be negative.

5) Consider the function $f(t) = (\max(0, t))^2$ for $-\infty < t < \infty$, where $\max(a, b)$ denotes the maximum of a and b . Which of the following statements is/are true?

(EE:2024)

- a) $f(t)$ is not differentiable.
b) $f(t)$ is differentiable and its derivative is continuous.
c) $f(t)$ is differentiable but its derivative is not continuous.
d) $f(t)$ and its derivative are differentiable.

6) Which of the following differential equations is/are nonlinear?

(EE:2024)

- a) $tx(t) + \frac{dx(t)}{dt} = t^2 e^t, \quad x(0) = 0$ c) $x(t) \cos t - \frac{dx(t)}{dt} \sin t = 1, \quad x(0) = 0$
b) $\frac{1}{2}e^t + x(t)\frac{dx(t)}{dt} = 0, \quad x(0) = 0$ d) $x(t) + e^{\left(\frac{dx(t)}{dt}\right)} = 1, \quad x(0) = 0$

7) For a two-phase network, the phase voltages V_p and V_q are to be expressed in terms of sequence voltages V_α and V_β as $\begin{pmatrix} V_p \\ V_q \end{pmatrix} = S \begin{pmatrix} V_\alpha \\ V_\beta \end{pmatrix}$. The possible option(s) for matrix S is/are

(EE:2024)

a) $\begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$

b) $\begin{pmatrix} 1 & 1 \\ 1 & 1 \end{pmatrix}$

c) $\begin{pmatrix} 1 & 1 \\ 1 & 0 \end{pmatrix}$

d) $\begin{pmatrix} -1 & 1 \\ 1 & 1 \end{pmatrix}$


- 8) Which of the following options is/are correct for the Automatic Generation Control (AGC) and Automatic Voltage Regulator (AVR) installed with synchronous generators?

(EE:2024)

- a) AGC response has a local effect on frequency while AVR response has a global effect on voltage.
- b) AGC response has a global effect on frequency while AVR response has a local effect on voltage.
- c) AGC regulates the field current of the synchronous generator while AVR regulates the generator's mechanical power input.
- d) AGC regulates the generator's mechanical power input while AVR regulates the field current of the synchronous generator.

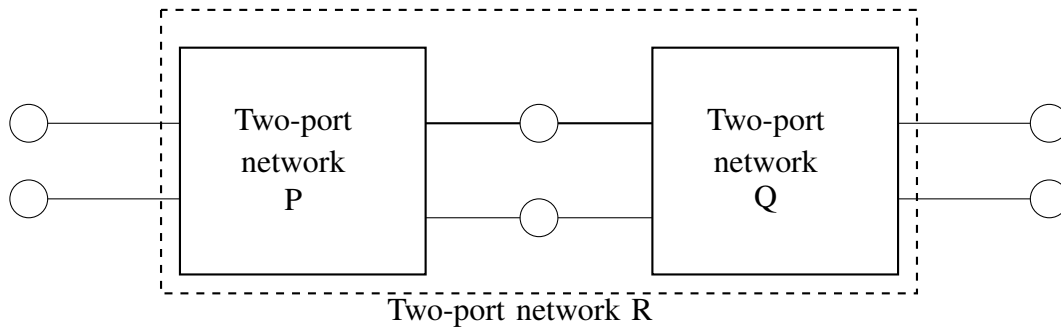
- 9) Two passive two-port networks **P** and **Q** are connected as shown in the figure. The impedance matrix of network **P** is $Z_P = \begin{pmatrix} 40\Omega & 60\Omega \\ 80\Omega & 100\Omega \end{pmatrix}$. The admittance matrix of network **Q** is $Y_Q = \begin{pmatrix} 5S & -2.5S \\ -2.5S & 1S \end{pmatrix}$.

Let the ABCD matrix of the two-port network **R** in the figure be $\begin{pmatrix} \alpha & \beta \\ \gamma & \delta \end{pmatrix}$. The value of β in Ω is _____ (rounded off to 2 decimal places).




(EE:2024)

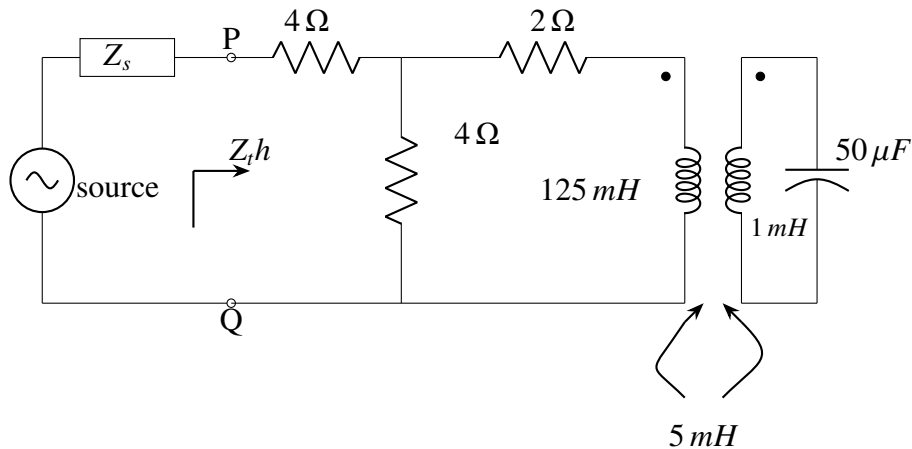- 10) For the circuit shown in the figure, the source frequency is 5000 rad/sec . The mutual inductance between the magnetically coupled inductors is 5 mH with their self inductances being 125 mH and 1 mH . The Thevenin's impedance, Z_{th} , between the terminals **P** and **Q** in Ω is _____ (rounded off to 2 decimal places).



(EE:2024)

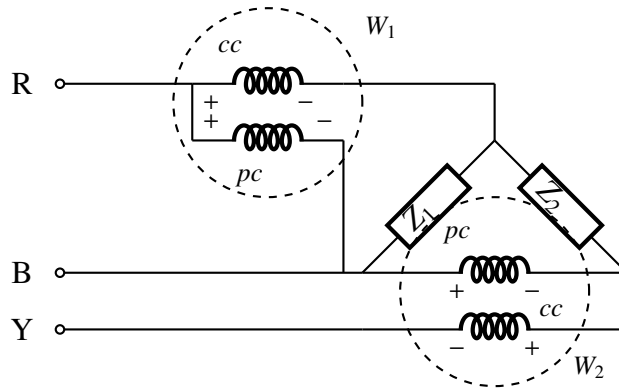- 11) In the circuit shown, $Z_1 = 50\angle -90^\circ \Omega$ and $Z_2 = 200\angle -30^\circ \Omega$. It is supplied by a three phase 400 V source with the phase sequence being R-Y-B. Assume the watt meters W_1 and W_2 to be ideal. The magnitude of the difference between the readings of W_1 and W_2 in watts is _____ (rounded off to 2 decimal places).



(EE:2024)

- 12) In the (x, y, z) coordinate system, three point-charges Q , Q , and αQ are located in free space at $(-1, 0, 0)$, $(1, 0, 0)$, and $(0, -1, 0)$, respectively. The value of α for the electric field to be zero at $(0, 0.5, 0)$ is _____ (rounded off to 1 decimal place).

(EE:2024)

- 13) The given equation represents a magnetic field strength $\mathbf{H}(r, \theta, \phi)$ in the spherical coordinate system, in free space. Here, \hat{r} and θ represent the unit vectors along r and θ , respectively. The value of P in the equation should be _____ (rounded off to the nearest integer).

$$\bar{H}(r, \theta, \phi) = \frac{1}{r^3} (\hat{r}P \cos \theta + \hat{\theta} \sin \theta)$$

(EE:2024)